



$$V_{rms} = \frac{V_p}{\sqrt{2}}$$

$$\frac{V_p}{V_s} = \frac{N_p}{N_s} = \sqrt{\frac{L_p}{L_s}}$$

$$\frac{L_p}{L_s} = \left(\frac{V_p}{V_s}\right)^2 = \left(\frac{230}{15}\right)^2$$

$$\frac{L_1}{L_2} = \frac{2116}{9}$$

for the rectifier bridge.

$$\begin{aligned} PIV &= V_p(sec) - 0.7 V \\ &= 15\sqrt{2} - 0.7 V \\ &= 20.5132 V \end{aligned}$$

$$\begin{aligned} V_p(out) &= V_p(sec) - 1.4 \\ &\approx 15\sqrt{2} - 1.4 \\ &= 19.8132 V \end{aligned}$$

\*We may get a peak voltage of 19.8 V across the filter capacitor C.

Ripple calculations.

$$V_{ripple} = \frac{I_{max}}{2fC}$$

$$I_{max} = 10 A \Rightarrow$$

$$V_{ripple} = \frac{10}{2 \times 100 C}$$

$$C = \frac{1}{20 V_{ripple}}$$

for  $C = 6800 \mu F$  (which is available in market) we may expect a ripple of around 7.35 V which is acceptable for our purpose.

## Calculations with Zener diode.

for the proper operation of Zener

$$I_K < I_Z < I_{max}$$

$$I_K < \frac{V_{in} - V_Z}{R_1} < I_{max}$$

$$\frac{I}{I_K} > \frac{R_1}{V_{in} - V_Z} > \frac{I}{I_{max}}$$

$$\frac{V_{in} - V_Z}{I_K} > R_1 > \frac{V_{in} - V_Z}{I_{max}}$$

$$R_1 < \frac{V_{in} - V_Z}{I_K} \quad \text{and} \quad \frac{V_{in} - V_Z}{I_{max}} < R_1$$

$$* \quad R_1 < \frac{(V_{in} - V_Z)_{min}}{I_K} \quad \text{and} \quad \frac{(V_{in} - V_Z)_{max}}{I_{max}} < R_1$$

$$R_1 < \frac{19.81 - 7.35 - V_Z}{I_K} \quad \text{and} \quad \frac{19.81 - V_Z}{I_{max}} < R_1 \quad \text{--- ②}$$

considering component availability and operating ranges we choose 1N4733A Zener diode for our circuit.

for 1N4733A Zener,

$$I_{ZK} = 1 \text{ mA}$$

$$I_{ZT} = 49 \text{ mA}$$

$$I_{ZM} = 178 \text{ mA} \quad (@ 50^\circ \text{C})$$

$$V_Z = 5.1 \text{ V}$$

$$\textcircled{1} \Rightarrow R_1 < \frac{12.46 - 5.1}{1 \times 10^{-3}}$$

$$R_1 < 7.36 \text{ k}\Omega \quad \text{and}$$

$$\textcircled{2} \Rightarrow \frac{19.81 - 5.1}{178 \times 10^{-3}} < R_1$$

$$R_1 > 82.64 \Omega$$

But to operate in test current (49 mA),

$$R_1 = \frac{(19.81 - V_{ripple} \times \frac{2}{3}) - V_Z}{49 \times 10^{-3}} = 200.2 \Omega \quad \text{is preferred.}$$

$Q_2$  and  $R_3$  are for over current protection.

We may forward bias the  $Q_2$  transistor when there is a current greater than 10 A to the load, to reduce the base current of  $Q_1$ , which will reduce the emitter current that is going through the load.

$$R_3 = \frac{0.7}{10} = 0.07 \Omega.$$

We can neglect the base current of feedback transistor  $Q_3$  and consider  $R_4$  and  $R_5$  resistors as potential dividers.

$$\frac{V_E + 0.7}{R_5} \times (R_4 + R_5) = 10 \text{ V}$$

$$\frac{R_4}{R_5} + 1 = \frac{10}{5.1 + 0.7} = \frac{10}{5.8}$$

$$\frac{R_4}{R_5} = \frac{4.2}{5.8}$$